

# **Chapter 4**

## **The Processor**

### **Lecture 8**

**Dr. Karim Emara**


# Agenda

---

- MIPS Revision
- Exercises


# R-Type Instruction

Instruction	RegDst	ALUSrc	MemtoReg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0

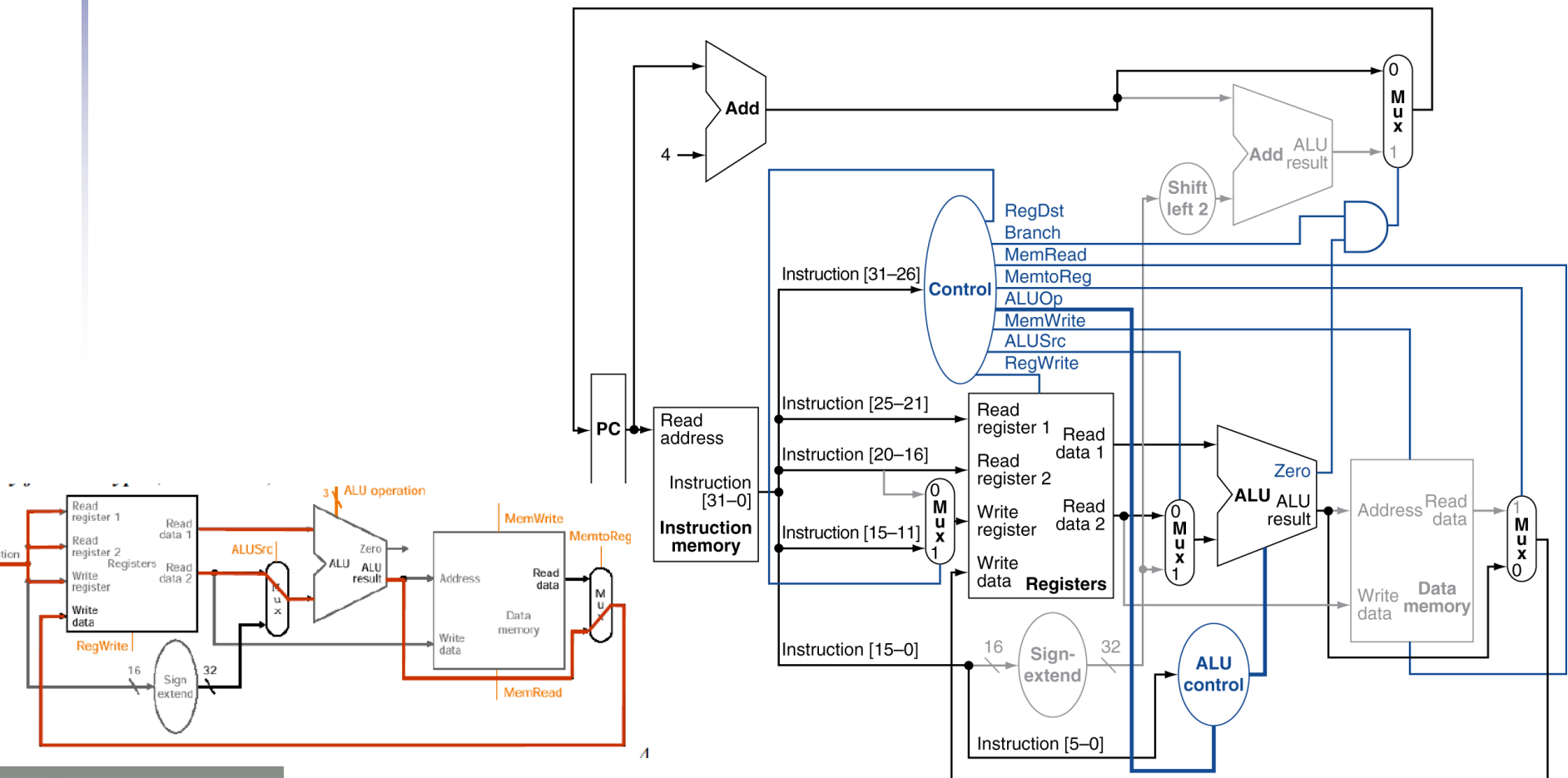


# Load Instruction


Instruction	RegDst	ALUSrc	MemtoReg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0

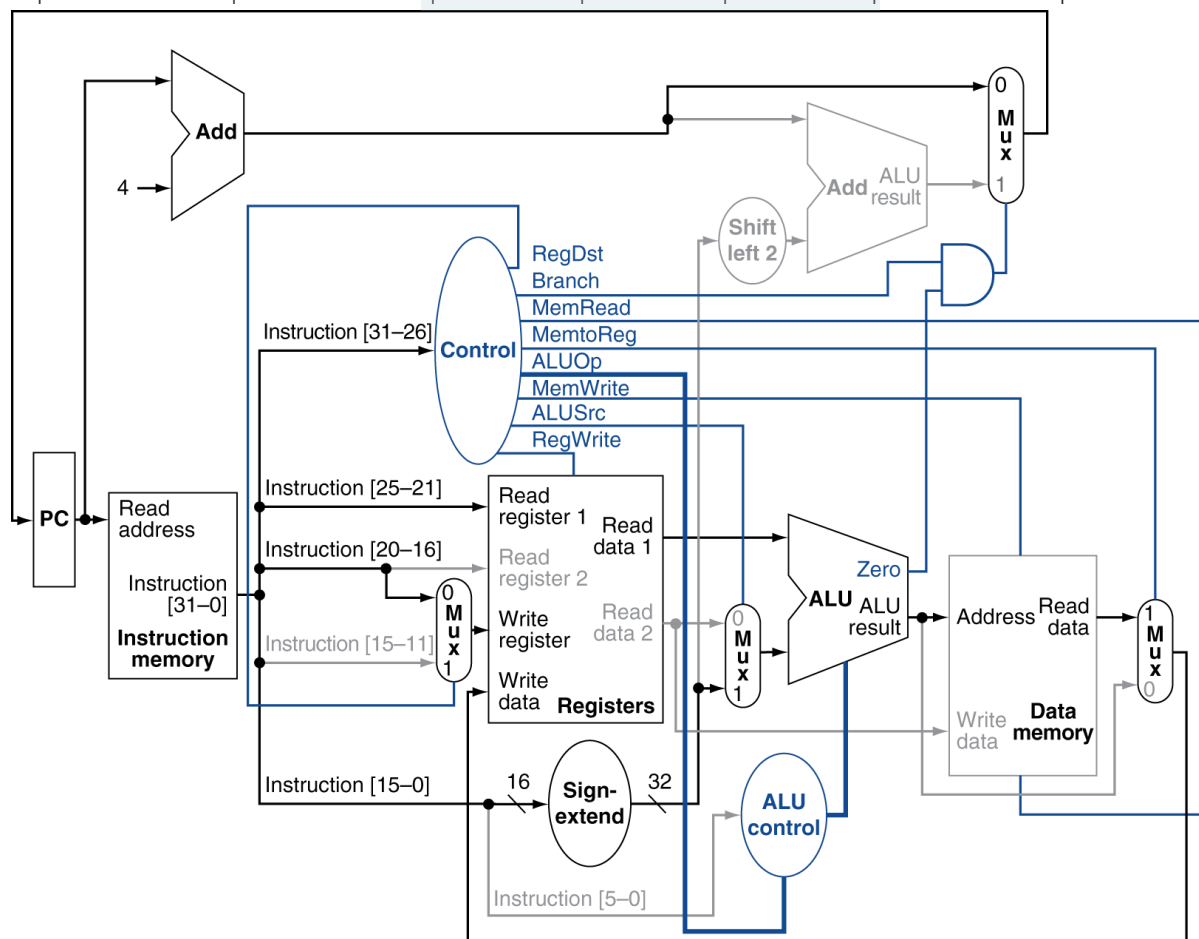

# Single Cycle MIPS

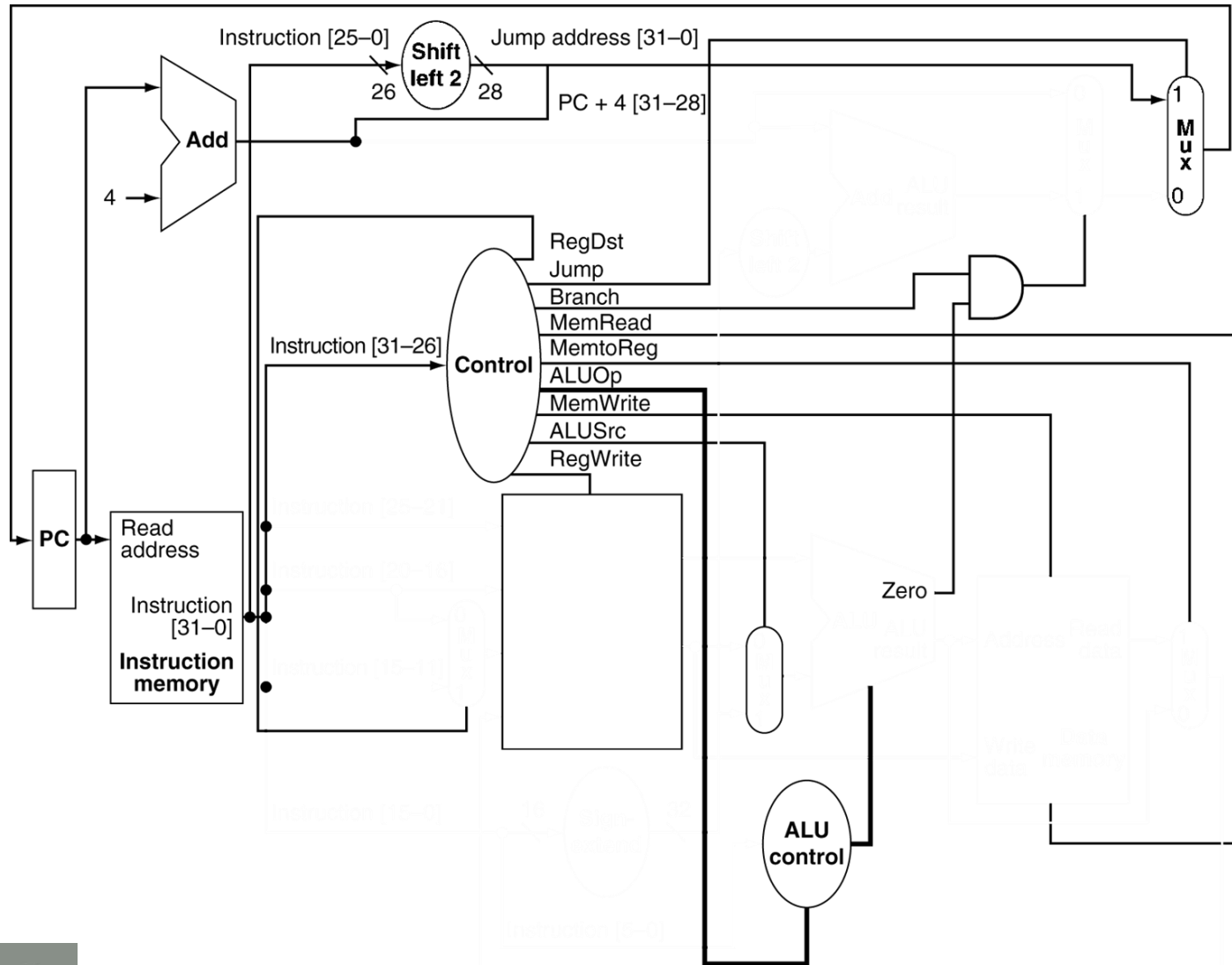

# Pipelined MIPS

 

# Agenda

---


- Pipelining Revision
- Exercises

# Exercise 4.3

- Assume that we are starting with a datapath from Figure 4.2, where I-Mem, Add, Mux, ALU, Regs, D-Mem, and Control blocks have **latencies** of 400 ps, 100 ps, 30 ps, 120 ps, 200 ps, 350 ps, and 100 ps, respectively,
- and **costs** of 1000, 30, 10, 100, 200, 2000, and 500, respectively.
- Consider the addition of a multiplier to the ALU. This addition will add 300 ps to the latency of the ALU and will add a cost of 600 to the ALU. The result will be 5% fewer instructions executed since we will no longer need to emulate the MUL instruction.



# Figure 4.2

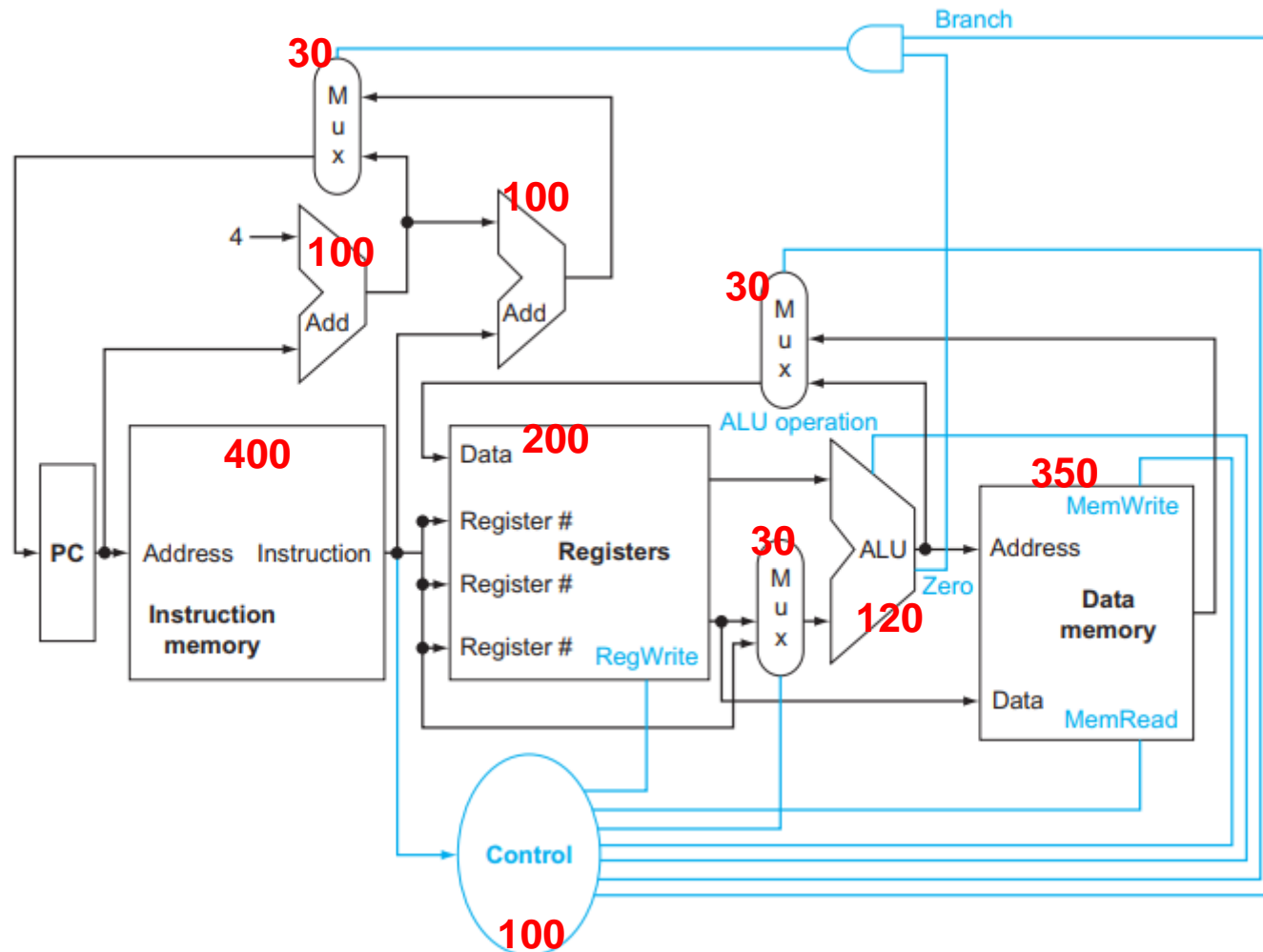

# Exercise 4.3.1

- What is the clock cycle time with and without this improvement?
- Clock cycle time is determined by the critical path (load instruction): I-Mem (read instruction), Regs (read registers and write data), Mux (select ALU input), ALU, Data Memory, and Mux (select value from memory to be written into Registers).

	I-MEM	Regs	Mux	ALU	D-Mem	Mux	
	Add	Control	Mux				
		Add					
W/O	400	200	30	120	350	30	=1130ps
Wt Improve	400	200	30	420	350	30	=1430ps

## Exercise 4.3.2

- What is the speedup achieved by adding this improvement?
- $\text{Speedup} = \text{CPU Time}_{\text{wo-imp.}} / \text{CPU Time}_{\text{w-imp.}}$
- $\text{CPU Time} = \# \text{ Cycles} \times \text{Cycle Time}$
- $S = 1.0 \text{ C} \times 1130 / 0.95 \text{ C} \times 1430$
- $= 0.83$  (**Slowdown**)

# Exercise 4.4.1

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps


- If the only thing we need to do in a processor is **fetch consecutive instructions** what would the cycle time be?
- Fetch requires I-MEM access and PC +4 (ADD)
- Both components run in parallel, so the cycle time =  $\max(\text{I-MEM}, \text{ADD}) = 200 \text{ ps}$

# Exercise 4.4.2

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

- Assume processor has only one type of instruction: **unconditional PC-relative branch**. What the cycle time?

# Single-Cycle MIPS

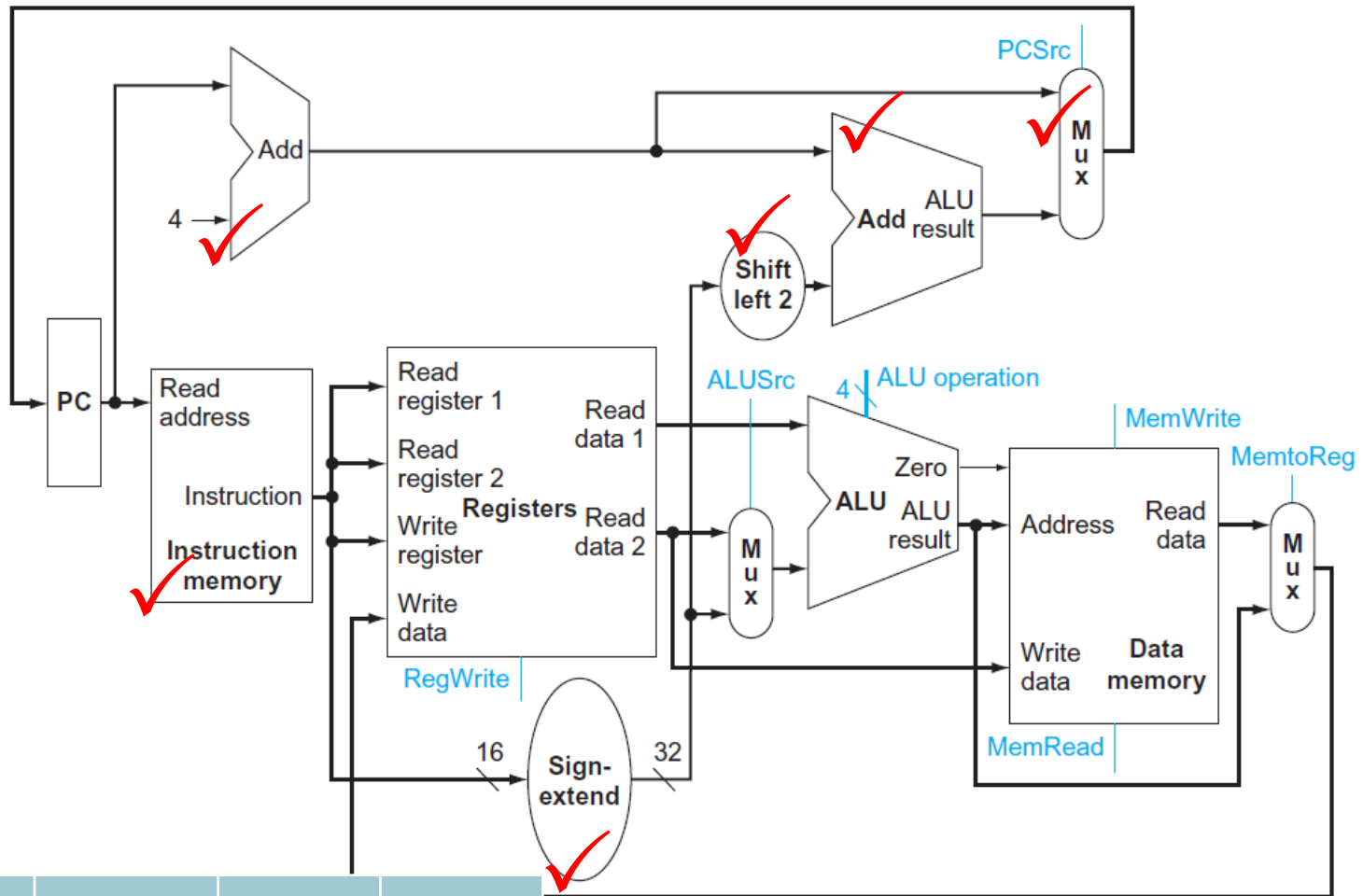

I-MEM	Sign	Shift 2	ADD	MUX
Add				

# Exercise 4.4.2

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

- The critical path for this instruction is:
- I-MEM, Sign-Extend, Shift-Left-2, Add, MUX
- Cycle time =  $200 + 15 + 10 + 70 + 20 = 315$  ps

# Exercise 4.4.3


I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

- Assume processor has only one type of instruction: **conditional PC-relative branch**. What the cycle time?



# Single-Cycle MIPS

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

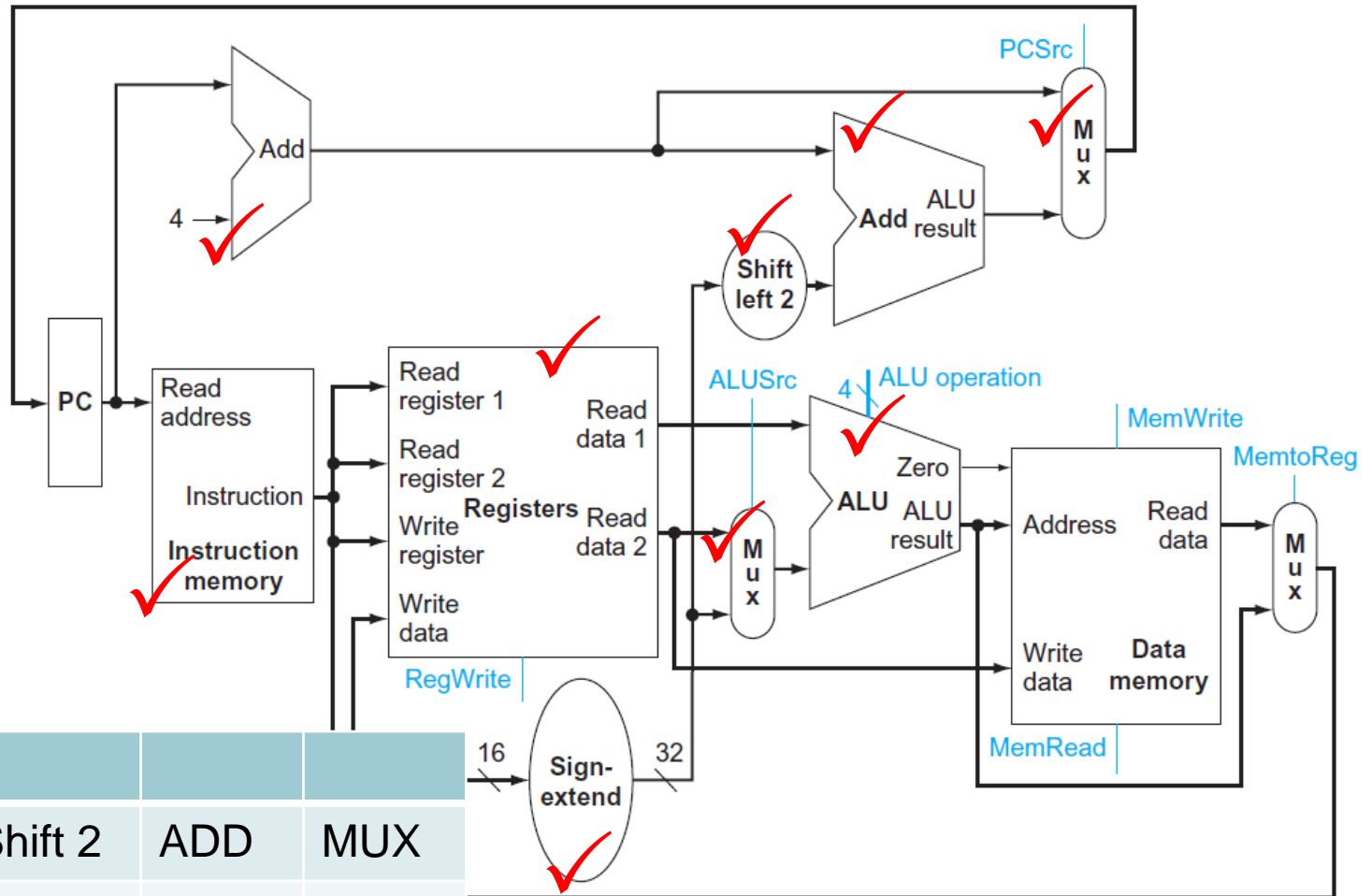

I-MEM	Sign	Shift 2	ADD	MUX
Add	Reg	MUX	ALU	

# Exercise 4.4.3

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

- The critical path for this instruction is:
- I-MEM, Regs, MUX, ALU, MUX (ignore the other parallel path of shorter delays)
- Cycle time =  $200 + 90 + 20 + 90 + 20 = 420$  ps

# Exercise 4.4.6

I-Mem	Add	Mux	ALU	Regs	D-Mem	Sign-Extend	Shift-Left-2
200ps	70ps	20ps	90ps	90ps	250ps	15ps	10ps

- Assuming that we only support **bne** and **add**, discuss how changes in **Shift-left-2** latency affect the cycle time of the processor.

BNE				
I-MEM	Sign	Shift 2	ADD	MUX
Add	Reg	MUX	ALU	

# Exercise 4.4.6

- Add instruction has shorter path than Bne. So it does not affect the cycle time
- In Bne, delay of the shift-left component is not included in the critical path of Bne execution
- Shift-left will make difference if its delay is increased so that **its path becomes the critical path**
- i.e.:  $(\text{SignExtend} + \text{ShiftLeft} + \text{Add}) > (\text{Regs} + \text{MUX} + \text{ALU})$
- $\text{ShiftLeft} > (90 + 20 + 90) - (15 + 70)$   
 $> 115\text{ps}$  (increased by 105ps more)

# Exercise 4.7

- instruction word: 101011 00011 00010 00000 00000010100.
- Assume that data memory is all zeros and that the processor's registers have the following value


r0	r1	r2	r3	r4	r5	r6	r8	r12	r31
0	-1	2	-3	-4	10	6	8	2	-16

- 101011 → sw, rs = 3, rt = 2, Imm = 20

## 4.7.1

- What are the outputs of the sign-extend and the jump “Shift left 2” unit for this instruction word?
- Sign-Extend: 0...000 00010100
- Jump Shift-left: 00011 00010 00000  
00000010100 **00**

# Single Cycle MIPS

 

## 4.7.2, 3

- What are the values of the ALU control unit's inputs for this instruction?
- ALU control = 00 → add
- What is the new PC address after this instruction is executed? Highlight the path through which this value is determined.
- $PC + 4$
- Path: Add (PC4) to branch Mux to jump Mux to PC



## 4.9

- Assume the following sequence of instructions:
- or r1,r2,r3
- or r2,r1,r4
- or r1,r1,r2
- Also, assume the following cycle times for each of the options related to forwarding

**Without Forwarding**

250ps

## 4.9.1

- Indicate dependences and their type.
- I2 and I3 depend on I1
- I3 depends on I2
- All dependencies cause data hazards

## 4.9.2

- Assume there is **no forwarding** in this pipelined processor. Indicate hazards and add nop instructions to eliminate them.

CC	1	2	3	4	5	6	7
I1	IF	ID R2, R3	EX	MEM	WB R1		
I2		IF	ID <b>R1</b> , R4	EX	MEM	WB R2	
I3			IF	ID <b>R1</b> , <b>R2</b>	EX	MEM	WB R1

Diagram illustrating instruction execution in a 5-stage pipeline (IF, ID, EX, MEM, WB) across 7 clock cycles (CC). Instruction I1 starts at CC1. Instruction I2 starts at CC2. Instruction I3 starts at CC3. A data hazard is indicated between I2 and I3, where I2's EX stage (CC4) writes to R1, which I3 needs in its ID stage (CC4). The hazard is resolved by inserting 2 CC of delay (nops) after I2's EX stage, shifting I3's ID stage to CC5.

## 4.9.2

- OR R1,R2,R3
- NOP
- NOP
- OR R2,R1,R4
- NOP
- NOP
- OR R1,R1,R2

# Reference

- Book sections: 4.1 – 4.6 (except parts not mentioned in the lectures)
- Exercises: 4.1 – 4.10 except 4.6